

## ORAL WORK N°2 ON CONDUCTORS

### PART 1

a) Complete the following :


If U against I graph of a conductor is a straight line passing through the origin, the conductor is a ..... one. An example is the .....

If U against I graph of a conductor is not a straight line but symmetrical about the origin, the conductor is a ..... - ..... one. An example is a .....

If U against I graph of a conductor is not a straight line and non - symmetrical about the origin, the conductor is a ..... - ..... one. An example is a .....


b) Sketch I against U graph of a diode.

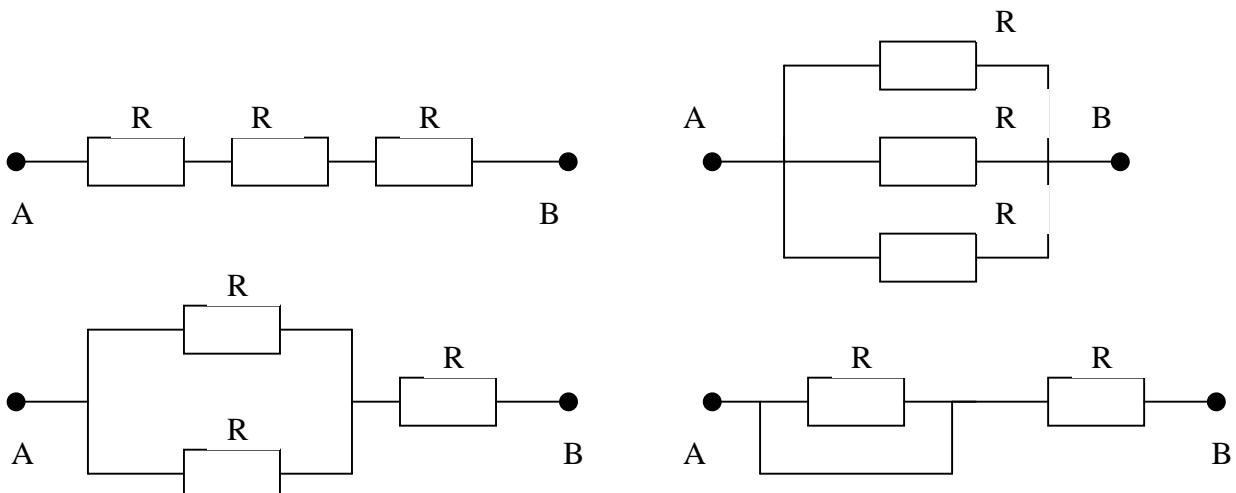c) Calculate the equivalent resistance of the following circuits with  $R = 1 \text{ k}\Omega$ .



## PART 2

The following circuit is given :

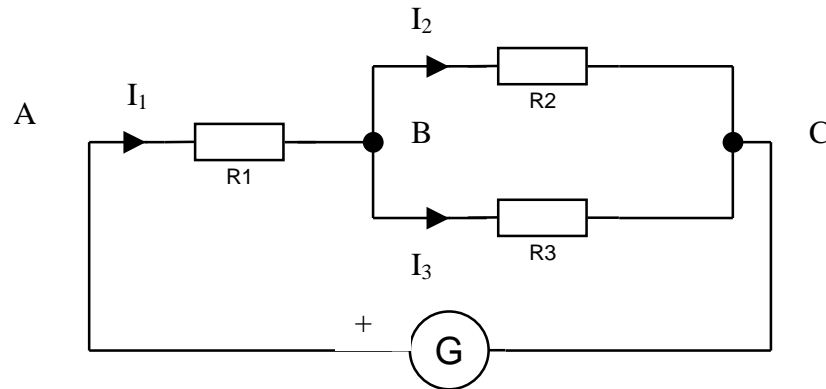

The generator delivers a constant voltage  $V_{AC} = 10 \text{ V}$ .  
 $R_1 = 75 \, \Omega$  ,  $R_2 = R_3 = 50 \, \Omega$ .

- Note  $V_{AB}$ ,  $V_{BC}$  and  $V_{AC}$  on the circuit.
- Calculate the equivalent resistance of the circuit.
- Apply Ohm's law to calculate  $I_1$ .
- Calculate the equivalent resistance of  $R_2$  and  $R_3$  and hence calculate  $V_{BC}$ .
- Calculate  $I_2$  and  $I_3$ .