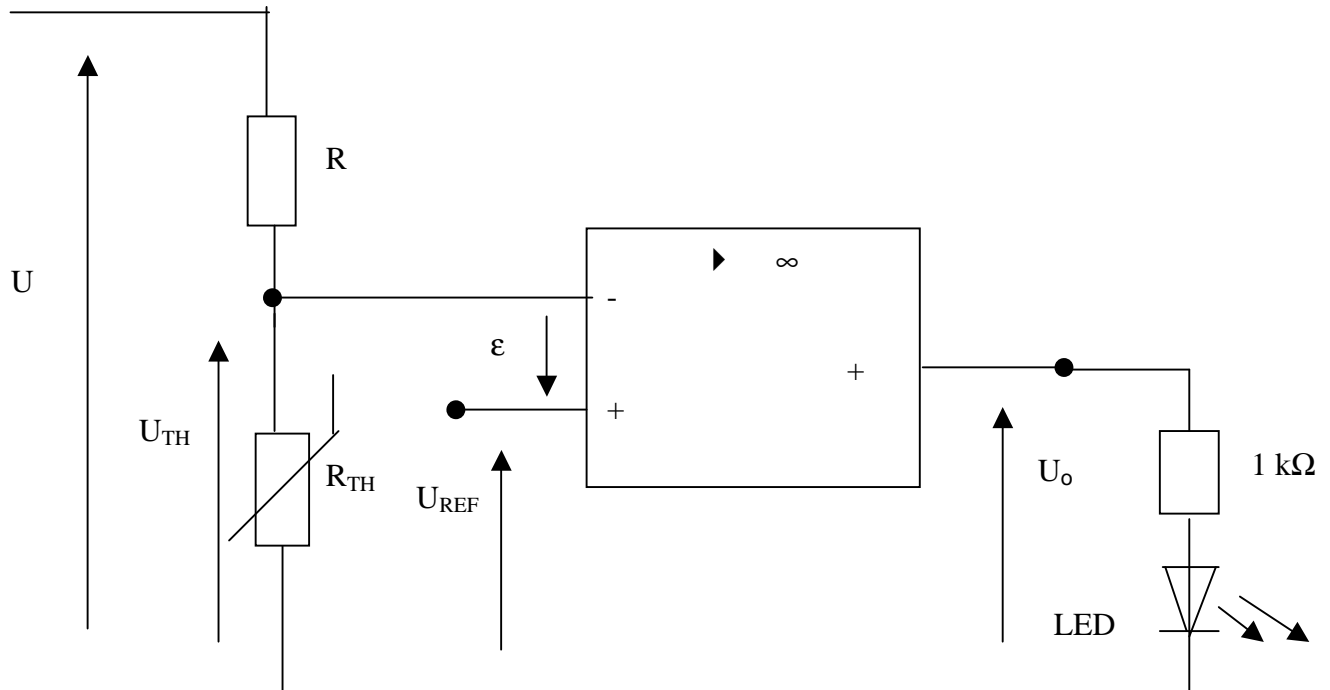


**ORAL WORK ON VOLTAGE COMPARATOR CIRCUIT****PART 1**

The following circuit is given:



$U = \text{constant voltage} = 10 \text{ V}$  ;  $U_{\text{REF}} = \text{reference voltage} = 3 \text{ V}$ ;


$R_{\text{TH}} = \text{resistance of a NTC type thermistor depending on temperature } \theta$ .

(The graph of  $R_{\text{TH}}$  against temperature  $\theta$  is given on page N°2)

The operational amplifier is supposed to be ideal and functions **non-linearly**:

Output voltage  $U_o$  can take 2 values  $+V_{\text{SAT}} = 15 \text{ V}$  and  $-V_{\text{SAT}} = -15 \text{ V}$ .

- Give  $\varepsilon$  in terms of  $U_{\text{REF}}$  and  $U_{\text{TH}}$ .
- Apply the voltage divider formula to give  $U_{\text{TH}}$  in terms of  $U$ ,  $R$  and  $R_{\text{TH}}$ .
- What is the value of  $R_{\text{TH}}$  when temperature  $\theta = 25 \text{ }^\circ\text{C}$  ? Calculate  $U_{\text{TH}}$  at this temperature.
- What is the value of  $R_{\text{TH}}$  when temperature  $\theta = 55 \text{ }^\circ\text{C}$  ? Calculate  $U_{\text{TH}}$  at this temperature.
- $U_{\text{TH}} = 5 \text{ V}$  at temperature  $\theta = 25 \text{ }^\circ\text{C}$ . Give the value of  $U_o$  and say whether the LED lights or not.
- $U_{\text{TH}} = 2.3 \text{ V}$  at temperature  $\theta = 55 \text{ }^\circ\text{C}$ . Give the value of  $U_o$  and say whether the LED lights or not.
- Give an application for the circuit.

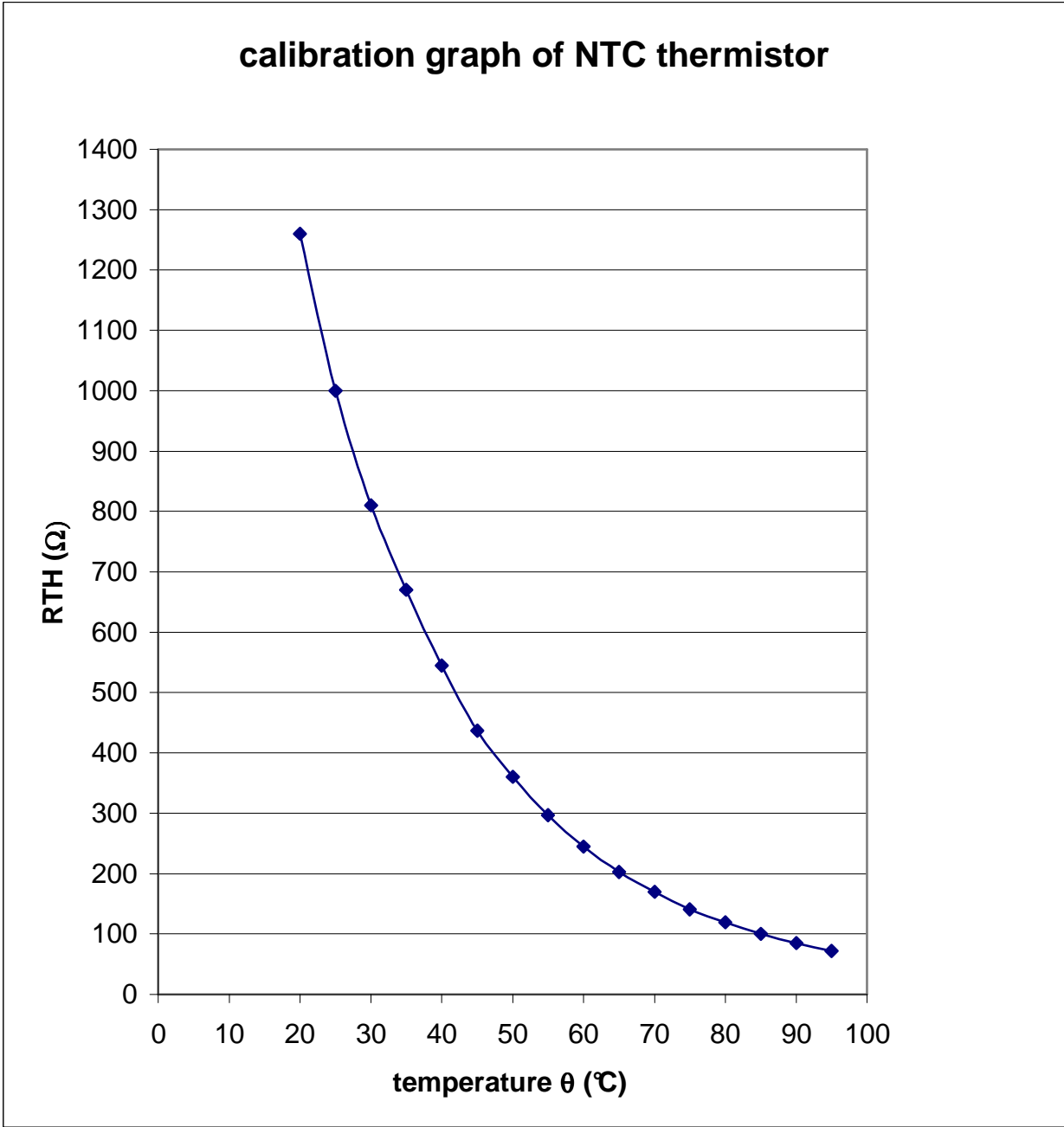

**PART 2****ABOUT SENSORS**


Sensors convert physical quantities into electric quantities. Sensors can depend on heat, light and strain.

An example of heat sensor is the thermistor whose resistance changes when temperature changes.

An example of light sensor is the light-dependent resistor (LDR) whose resistance changes when the intensity of light falling on it changes.

An example of strain sensor is the strain gauge which converts mechanical strain into a resistance change.

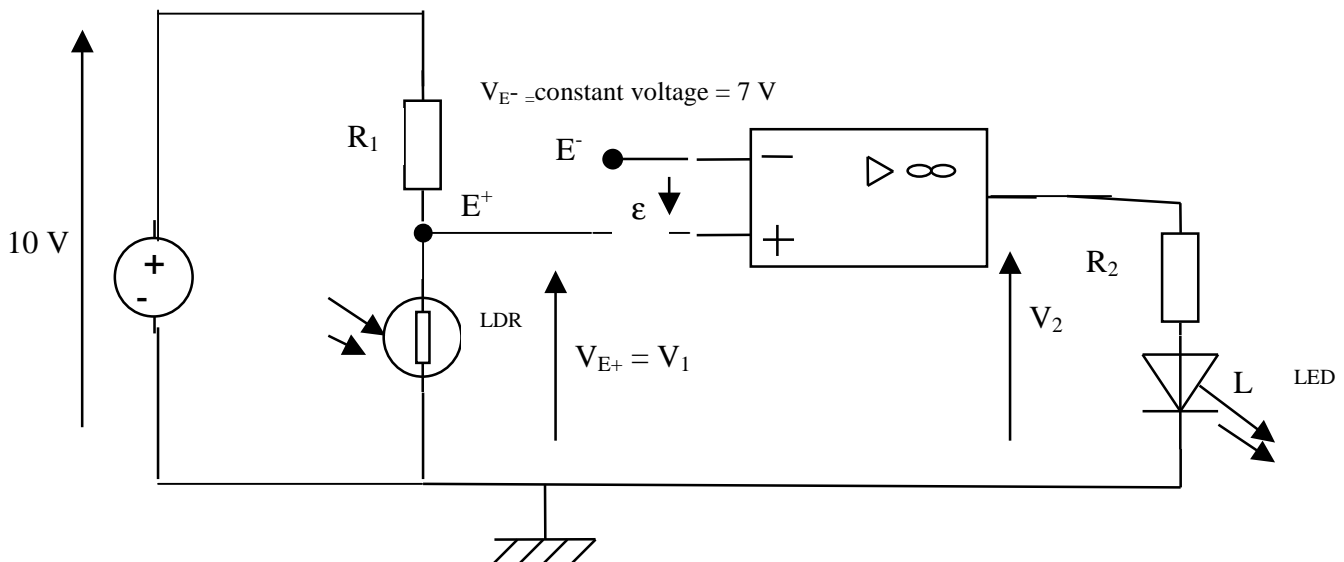We are going to consider a light-dependent resistor associated to a voltage comparator circuit



In presence of light the resistance of the LDR is equal to  $1\text{ k}\Omega$  and in absence of light the resistance of the LDR is equal to  $10\text{ M}\Omega$ .

The LED and op amp are supposed to be ideal. The op amp uses a symmetrical DC power supply  $= \pm V_{CC} = \pm 15\text{ V}$  and  $R_1 = R_2 = 1\text{ k}\Omega$ .

**PART 1 ( study of the LDR circuit)**

- The op amp being ideal, how are the LDR and  $R_1$  connected ?
- Apply the voltage divider formula to calculate  $V_1$  in the presence of light.
- Apply the voltage divider formula to calculate  $V_1$  in the absence of light.

**PART 2 ( study of the voltage comparator circuit)**

- Give the names of the 2 inputs  $E^+$  and  $E^-$  of the op amp.
- Does the op amp function linearly or non – linearly ? Explain why.
- Give the 2 possible values of  $V_2$ .

g) Give  $\varepsilon$  in terms  $V_{E+}$  and  $V_{E-}$ .

We assume that  $V_1 = 5 \text{ V}$  or  $10 \text{ V}$ .

h) Give the utility of resistance  $R_2$ .

i) When  $V_1 = 5 \text{ V}$  the LED does not light. Explain why.

j) When  $V_1 = 10 \text{ V}$  the LED lights. Explain why.

k) Give an application for the circuit.