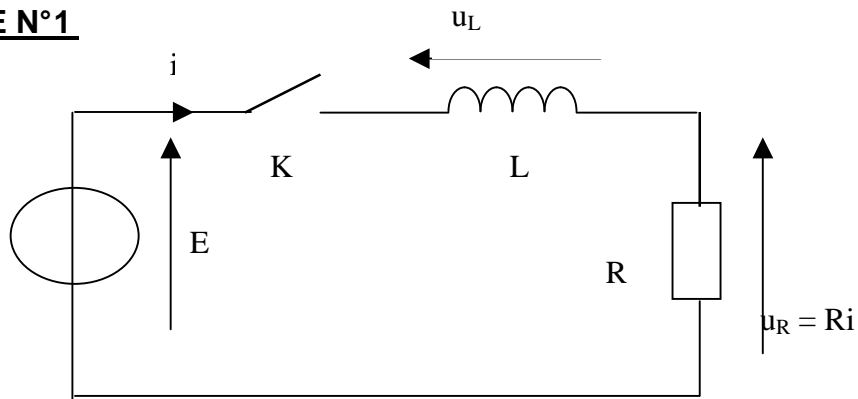


**ORAL WORK ON R-L CIRCUIT**

**EXERCISE N°1**




**E = DC voltage = 10 V, L = 1 H and R = 10 Ω.**

A  $t = 0$ , we close K.

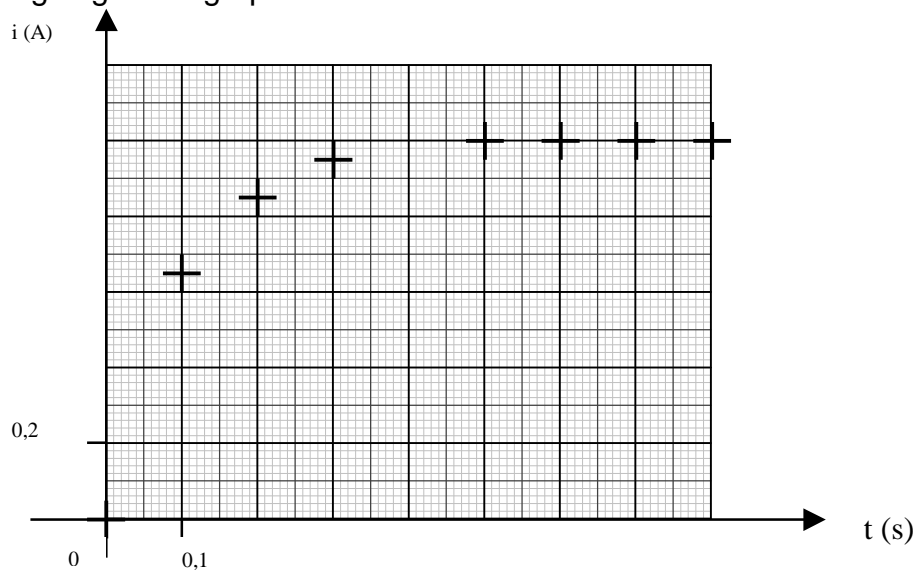a) Give the value of  $i$  when K is open.

The following  $i$  against  $t$  graph is obtained :



b) The value of  $i$  is still equal to 0 just after K is closed ( $t = 0^+$ ). Why ?

c) Calculate time constant  $\tau$  of the circuit.

d) Give the value of  $i$  at  $t = \tau$  and  $t = 3\tau$ .

e) Write the relationship between  $E$ ,  $u_L$  and  $u_R$ .

f) By writing Ohm's law for L and R. Show that the following equation is obtained :

$$\frac{di}{dt} + \frac{R}{L}i = \frac{E}{L}$$


g) Give the name of the equation.

h) We can show that the solution of the above equation is :

$$i = A + Be^{-\frac{t}{\tau}} \text{ where } \tau = \frac{L}{R}$$

Calculate A and B.

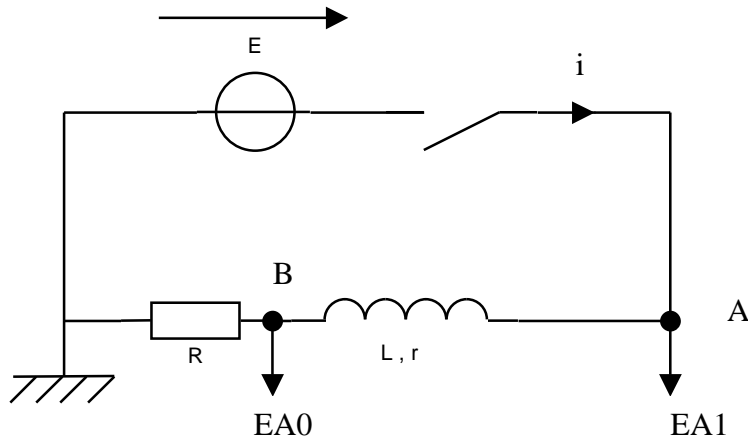
**EXERCISE N°2 (Extract from a baccalauréat subject)**



An electric circuit is composed of an ideal voltage source  $E = 10 \text{ V}$ , a switch  $K$ , an inductor  $L$  with a resistance  $r$  (real inductor) and a resistance  $R = 80 \Omega$ .

At  $t = 0 \text{ s}$ ,  $K$  is closed.

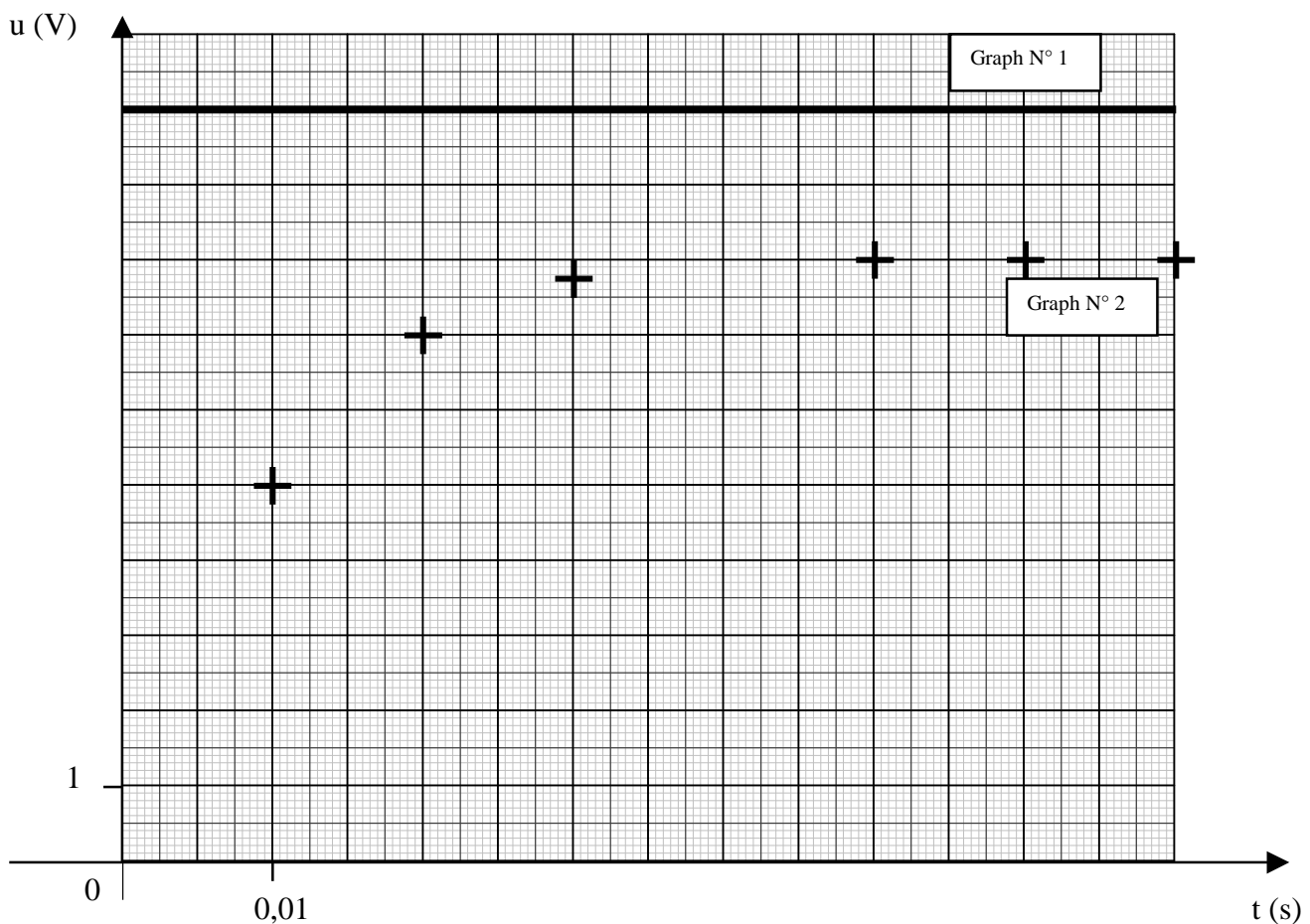A computer connected to the circuit with an appropriate interface gives the following graphs at channels  $EA0$  and  $EA1$ .



- Give the names of voltages at  $EA0$  and  $EA1$ .
- Associate each graph to each voltage.
- One of the voltage give the image of current  $i$ . Which one? Justify your answer;
- What influence has the inductor on current  $i$  ?

- e) Give the value of  $i$  at steady state. ( that is when  $i$  reaches its maximum value)
- f) By applying KVL calculate voltage  $v_{AB}$  across the inductor at steady state.
- g) Give  $v_{AB}$  in terms of  $r$ ,  $L$  and  $i$  and hence calculate the value of  $r$  at steady state  
knowing that  $L \frac{di}{dt} = 0$  at steady state.
- h) Express time constant  $\tau$  of the circuit and determine graphically its value.
- i) Determine the value of  $L$ .