
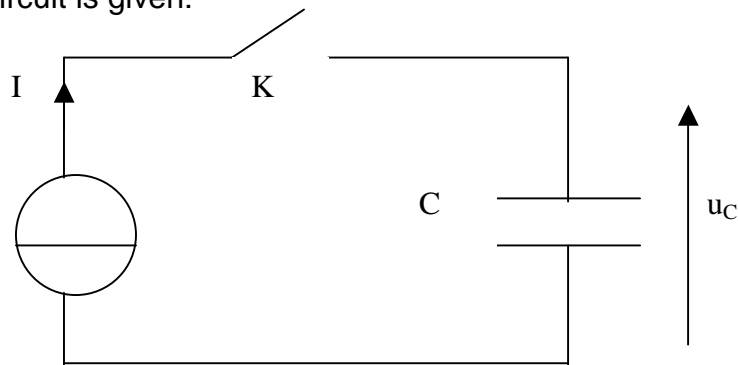


**ORAL WORK ON CONSTANT CURRENT CHARGE OF A CAPACITOR**

The following circuit is given:

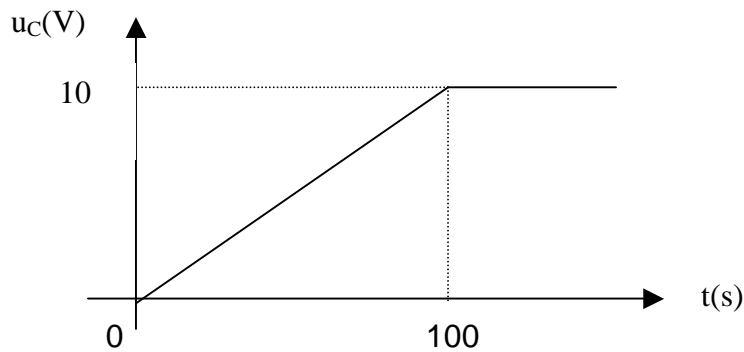

$I = 100 \mu\text{A} = \text{constant}$ ,  $C = 1000 \mu\text{F}$  and at  $t = 0$ ,  $K$  is closed.  
 $u_C$  is measured every 10 s for 100 s and at  $t = 100$  s,  $K$  is opened.  
 The following graph is obtained:



- Give the name of the source applied to the capacitor.
- Is the capacitor initially charged? Why?
- Give the relation between  $u_C$  and  $t$  for the straight line.
- Give the value of  $u_C$  when  $t = 30$  s.
- Calculate the charge  $q$  stored by the capacitor when  $t = 100$  s.
- The charged capacitor  $C = 1000 \mu\text{F}$  is isolated and connected in parallel with another discharged capacitor  $C' = 470 \mu\text{F}$ . Calculate the new voltage  $u'_C$  across them. ( hint : the value of  $q$  in question (e) remains constant)