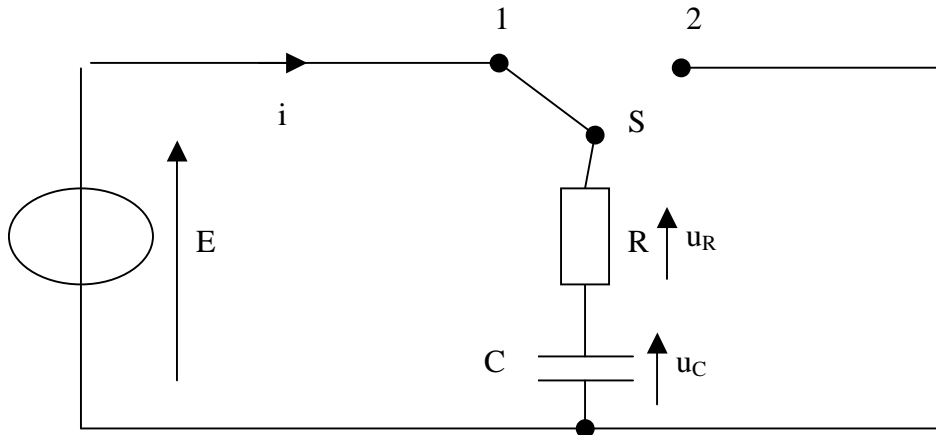


**PART 1 : CHARGE AND DISCHARGE OF CAPACITOR ACROSS R**


The following circuit is given:



$E$  is a constant voltage source and  $R = 12 \text{ M}\Omega$

By using switch  $S$ , the capacitor may be isolated from the voltage source and then discharged. Readings of the potential difference  $u_C$  across the capacitor are taken at regular intervals as the capacitor is charged and then discharged.

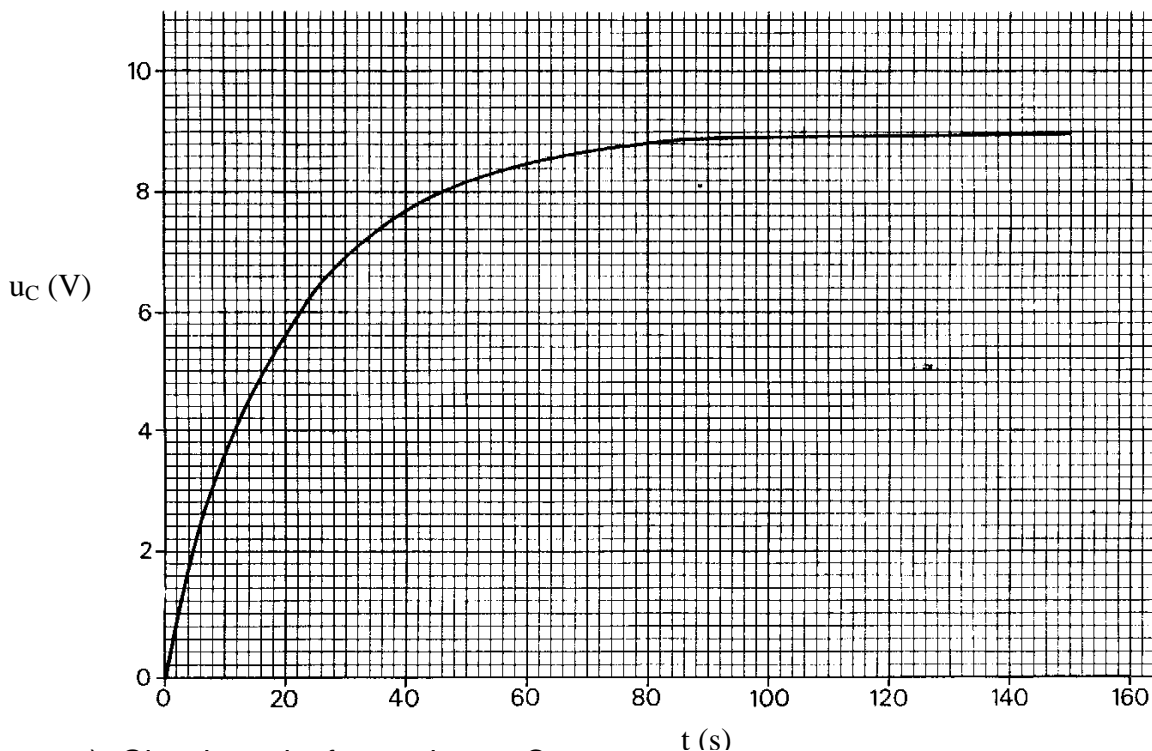When the switch  $S$  is on the **position 1** the following graph is obtained:



- Give the unit of capacitance  $C$ .
- State whether the graph represents the charge or the discharge of the capacitor.
- Is it a constant voltage charge across  $R$  or a constant current charge ?
- From the graph, deduce the value of voltage  $E$ .
- Express time constant  $\tau$  in terms of  $R$  and  $C$ .
- Give the % of charge after time  $t = \tau$  and deduce the value of capacitance  $C$ .
- What is the time taken by the capacitor to be charged at 95 %?

h) Apply KVL to show that the differential equation for the charge circuit is :

$$RC \frac{du_C}{dt} + u_C = E$$

i) We can show that the solution of the differential equation is :


$$u_C = E(1 - e^{-\frac{t}{\tau}})$$

Give the value of  $u_C$  when  $t$  tends to infinity and what is the mathematical name for  $E$  on the charge graph.

j) Sketch the graph of  $u_C$  against time when the switch is on **position 2.**

**PART 2 : ASTABLE CIRCUIT**


The following circuit is given :

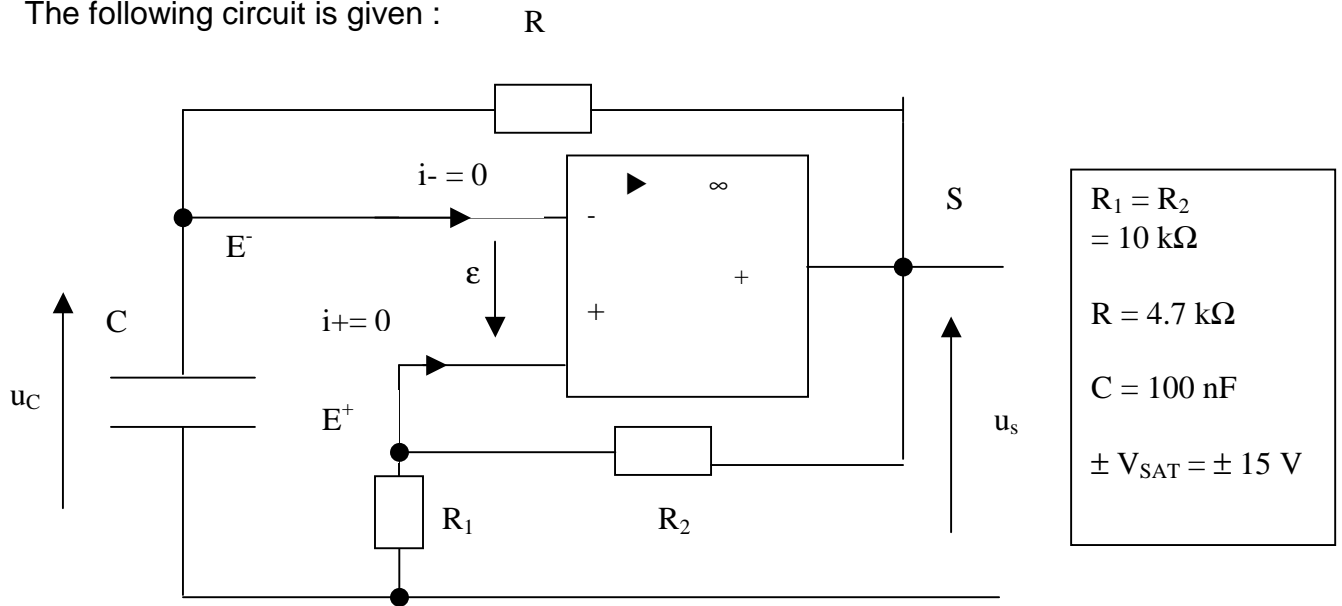

The **op amp** is supposed to be **ideal** and **functioning non-linearly**. Voltage  $u_S$  is a periodic signal of period  $T$ .

- What are the names of  $E^-$ ,  $E^+$  and  $S$  ?
- Give the 2 possible values of  $u_S$ .
- Apply the voltage divider formula to show that  $V_{E^+}$  can take 2 values  $\pm 7.5$  V.
- Express  $\epsilon$  in terms of  $V_{E^+}$  and  $u_C$ .
- Give the value of  $u_S$  if  $V_{E^+} > u_C$ .
- Give the value of  $u_S$  if  $V_{E^+} < u_C$ .

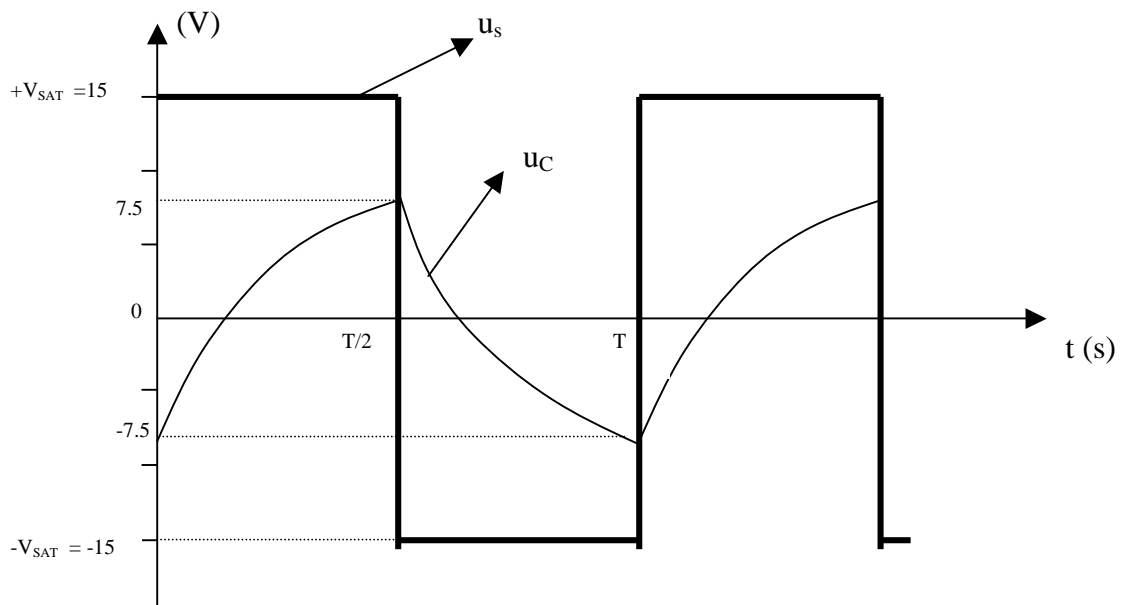The waveforms of  $u_S$  and  $u_C$  are given.



- g)  $u_S = +V_{SAT}$  for  $0 < t < T/2$ . What happens to the capacitor during this time?
- h) What is the maximum value of voltage  $u_C$  ?
- i) At time  $t = T/2$ ,  $\varepsilon = 0$ . What happens to voltage  $u_S$  ?
- j)  $u_S = -V_{SAT}$  for  $T/2 < t < T$ . What happens to the capacitor during this time?
- k) What is the minimum value of voltage  $u_C$  ?
- l) Give an application for the circuit.