




ORAL WORK ON RLC CIRCUIT : PART 1

A capacitor $C = 1 \mu\text{F}$ is charged at constant voltage E .

3 different circuits can be connected to the charged capacitor :

- ☞ an inductor L of negligible resistance ($r = 0 \Omega$)
- ☞ an inductor L with a resistance r
- ☞ a resistor of resistance R

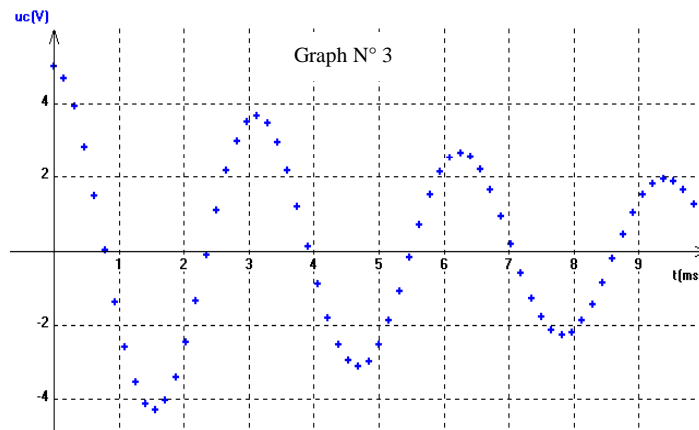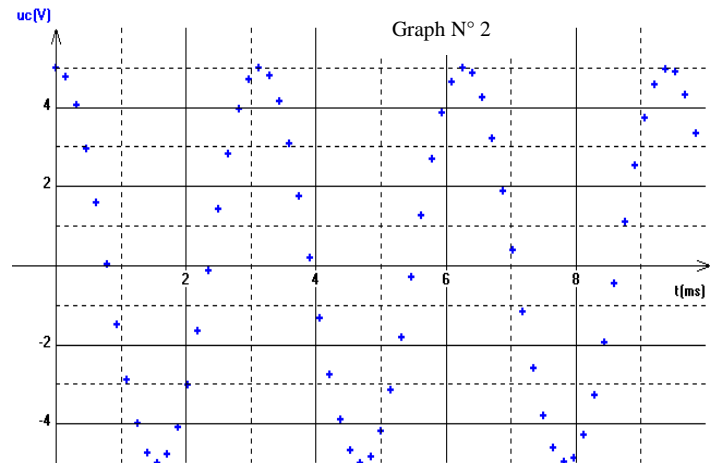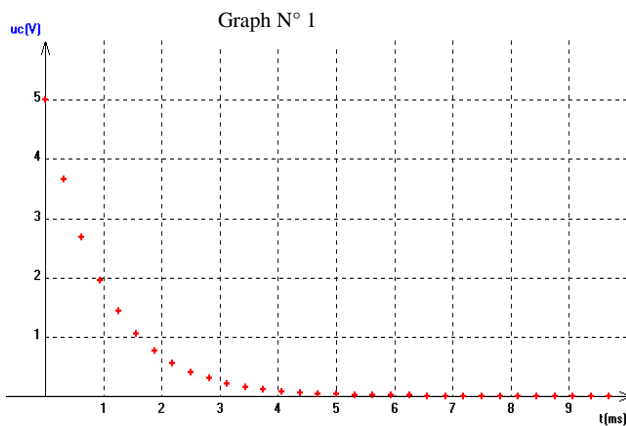
The following 3 graphs showing the variation of voltage u_C across the capacitor against time t are given :



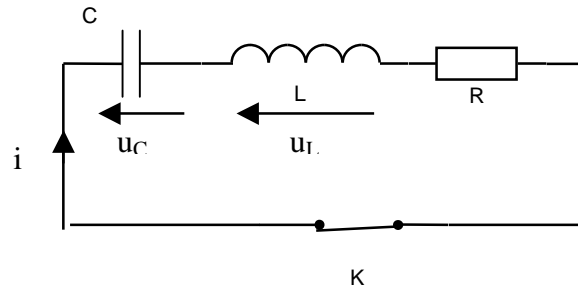- a) Associate each graph to each circuit. Give each time the reason of your choice.
- b) Which graph will enable us to calculate time constant τ ? Calculate τ and hence calculate the value of R .
- c) Which graph will enable us to calculate period T of oscillations ? Calculate T and hence calculate the value of L .
- d) Draw the circuit which correspond to each graph. Voltages and current i must appear on each circuit.
- e) Write down the differential equation for each circuit.
- f) Examine the case when the capacitor discharges in the inductor L of negligible resistance. Calculate the energy of the system at $t = 0$ and explain energy exchange between the capacitor and the inductor.
- g) Examine the case when the capacitor discharges in the inductor L of resistance r . Explain energy exchange between the capacitor and the inductor.


ORAL WORK ON RLC CIRCUIT (Extract BAC 2006): PART 2

We study free oscillations at a frequency $f_0 = 40$ kHz in the following circuit:



The capacitor C is initially charged at 4 V, $L = 1$ mH and the total resistance of the circuit is R

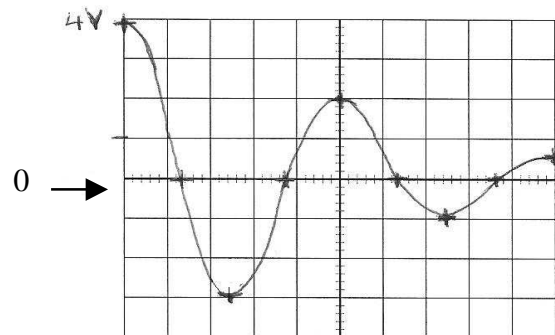
At $t = 0$ K is closed and a memory oscilloscope gives the following u_C against time graph :



Horizontal sensibility : 5 μ s/div

- What type of oscillations do we observe on the oscilloscope ?
- Discuss energy exchange in the circuit and explain why the oscillations are damped.
- How can we avoid damped oscillations knowing that R can never be 0 ?
- Say whether the following affirmations are true or false. Justify each time your answer.
 - ☞ Affirmation N° 1 : If we increase resistance R we shall always observe damped oscillations.
 - ☞ Affirmation N° 2 : Period T_0 of oscillations depend on initial value of u_C .
- Calculate T_0 from the graph and hence calculate the value of capacitance C of the capacitor.

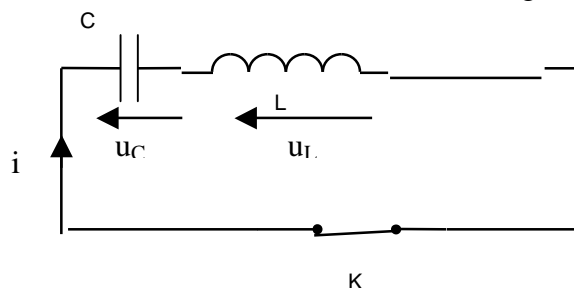We are going to consider now that $R = 0$ and the following circuit is obtained :



- Show that the differential equation is : $\frac{d^2 u_C}{dt^2} + \frac{1}{LC} u_C = 0$